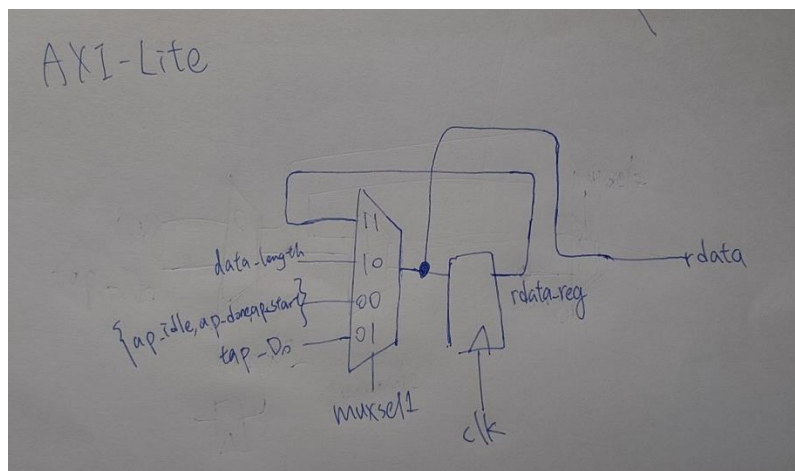




### Block Diagram

- 
- The diagram illustrates a 32-bit accumulator (acc) circuit. It features several inputs and outputs:
- Inputs:**
    - `data-D0`: A 32-bit data input.
    - `tap-D0`: A 32-bit tap input.
    - `acc-reset`: A reset signal.
    - `stall`: A stall signal.
    - `clk`: A clock signal.
  - Logic Components:**
    - A 32-bit multiplexer (MUX) selects between `data-D0` and `tap-D0` based on the condition `tap.idx > data.idx`. The output is multiplied (`X`) by a constant `0`.
    - The result is then added (`+`) to the current value of the accumulator (`acc`).
    - The accumulator is a 32-bit register that updates its value on the clock (`clk`) edge.
  - Outputs:**
    - `sm_tdata`: The output of the accumulator, which is also fed back into the `acc` input.
    - `acc`: The current value of the accumulator, which is also fed back into the `+` input.




- [illegible]

  - **How to receive data-in and tap parameters and place into SRAM**



fir 在讀入資料的同時會直接將資料寫入 SRAM

 - **How to access shiftram and tapRAM to do computation**



為了能增加 performance，不直接 shift SRAM 裡面的資料，而是移動每次開始讀取 data ram 的位置。而且在需要進行計算的前一個 cycle 就先將所需資料的位置給 SRAM，到下一個 cycle 時，除了對 SRAM 傳來的資料進行計算外，也將下一 cycle 所需資料的位置給 SRAM，如此可以充分利用資源。

- **How each output y is computed.**

計算一個 y 需要 11 個 clock cycle，tap\_idx 從 9 到 10。

9: 計算 tap10。開始計算一個新的 y，acc\_reset=1，重新累加

8~1: 計算 tap9~2

0: 計算 tap1。讀入一個 input x，並將其寫到 data ram

10: 計算 tap0。輸出 y，sm\_tvalid=1

對於前 11 個 y，因為 data ram 中的數值並未經過初始化，tap\_idx>data\_idx 來判斷要從 data ram 中讀取數值，還是直接用 0 進行計算

- **How ap\_done is generated.**

當最後一筆輸出被 fir\_tb 接收後將 ap\_done 設為 1

**Resource usage: including FF, LUT, BRAM**

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	303	0	0	53200	0.57
LUT as Logic	303	0	0	53200	0.57
LUT as Memory	0	0	0	17400	0.00
Slice Registers	145	0	0	106400	0.14
Register as Flip Flop	145	0	0	106400	0.14
Register as Latch	0	0	0	106400	0.00
F7 Muxes	0	0	0	26600	0.00
F8 Muxes	0	0	0	13300	0.00

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

從合成報告截圖中可以看出此設計並未使用 BRAM

## Timing Report

- Try to synthesize the design with maximum frequency

Clock Summary			
Clock	Waveform(ns)	Period(ns)	Frequency(MHz)
axis_clk	{0.000 5.000}	12.000	83.333

經過測試最短週期設為 12ns

- Report timing on longest path, slack

From Clock: axis_clk					
To Clock: axis_clk					
Setup :	0	Failing Endpoints, Worst Slack	0.269ns, Total Violation	0.000ns	
Hold :	0	Failing Endpoints, Worst Slack	0.132ns, Total Violation	0.000ns	
PW :	0	Failing Endpoints, Worst Slack	4.500ns, Total Violation	0.000ns	

## Max Delay Paths

```


Slack (MET) : 0.269ns (required time - arrival time)
Source: mul_data_in_sel_reg/C
              (rising edge-triggered cell FDRF clocked by axis_clk {rise@0.000ns fall@5.000ns period=12.000ns})
Destination: acc_reg[29]/D
              (rising edge-triggered cell FDRF clocked by axis_clk {rise@0.000ns fall@5.000ns period=12.000ns})
Path Group: axis_clk
Path Type: Setup (Max at Slow Process Corner)
Requirement: 12.000ns (axis_clk rise@12.000ns - axis_clk rise@0.000ns)
Data Path Delay: 11.626ns (logic 8.472ns (72.868%) route 3.154ns (27.132%))
Logic Levels: 10 (CARRY4=5 DSP48E1=2 LUT2=2 LUT4=1)
Clock Path Skew: -0.145ns (DCD - SCD + CPR)
Destination Clock Delay (DCD): 2.128ns ( 14.128 - 12.000 )
Source Clock Delay (SCD): 2.456ns
Clock Pessimism Removal (CPR): 0.184ns
Clock Uncertainty: 0.035ns ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE
Total System Jitter (TSJ): 0.071ns
Total Input Jitter (TIJ): 0.000ns
Discrete Jitter (DJ): 0.000ns
Phase Error (PE): 0.000ns

```

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
(clock axis_clk rise edge)				
		0.000	0.000 r	
net (fo=0)		0.000	0.000 r	axis_clk (IN)
		0.000	0.000	axis_clk
			r	axis_clk_IBUF_inst/I
IBUF (Prop_ibuf_l_0)		0.972	0.972 r	axis_clk_IBUF_inst/O
net (fo=1, unplaced)		0.800	1.771	axis_clk_IBUF
			r	axis_clk_IBUF_BURF_inst/I
BURF (Prop_burf_l_0)		0.101	1.872 r	axis_clk_IBUF_BURF_inst/O
net (fo=145, unplaced)		0.584	2.456	axis_clk_IBUF_BURF
FDRF			r	mul_data_in_sel_reg/C
-----				
FDRF (Prop_fdrf_C_Q)		0.478	2.934 f	mul_data_in_sel_reg/Q
net (fo=32, unplaced)		0.382	3.316	mul_data_in_sel
			f	acc2_0_i_1/I
LUT2 (Prop_lut2_l1_0)		0.295	3.611 r	acc2_0_i_1/O
net (fo=1, unplaced)		0.800	4.411	acc3[16]
			r	acc2_0/O[16]
DSP48E1 (Prop_dsp48e1_A[16]_PCOUT[47])		4.036	8.447 r	acc2_0/PCOUT[47]
net (fo=1, unplaced)		0.055	8.502	acc2_0_n_106
			r	acc2_1/PCIN[47]
DSP48E1 (Prop_dsp48e1_PCIN[47]_P[0])		1.518	10.020 r	acc2_1/P[0]
net (fo=2, unplaced)		0.800	10.820	acc2_1_n_105
			r	sm_tdata_OBUF[19]_inst_i_13/I
LUT2 (Prop_lut2_l0_0)		0.124	10.944 r	sm_tdata_OBUF[19]_inst_i_13/O
net (fo=1, unplaced)		0.000	10.944	sm_tdata_OBUF[19]_inst_i_13_n_0
			r	sm_tdata_OBUF[19]_inst_i_10/S[1]
CARRY4 (Prop_carry4_S[1]_CO[3])		0.533	11.477 r	sm_tdata_OBUF[19]_inst_i_10/CO[3]
net (fo=1, unplaced)		0.009	11.486	sm_tdata_OBUF[19]_inst_i_10_n_0
			r	sm_tdata_OBUF[23]_inst_i_10/CI
CARRY4 (Prop_carry4_CI_CO[3])		0.117	11.603 r	sm_tdata_OBUF[23]_inst_i_10/CO[3]
net (fo=1, unplaced)		0.000	11.603	sm_tdata_OBUF[23]_inst_i_10_n_0
			r	sm_tdata_OBUF[27]_inst_i_10/CI
CARRY4 (Prop_carry4_CI_O[3])		0.331	11.934 r	sm_tdata_OBUF[27]_inst_i_10/O[3]
net (fo=3, unplaced)		0.636	12.570	sm_tdata_OBUF[27]_inst_i_10_n_4
			r	acc[24]_i_2/I
LUT4 (Prop_lut4_l0_0)		0.307	12.877 r	acc[24]_i_2/O
net (fo=1, unplaced)		0.473	13.350	in[27]
			r	acc_reg[24]_i_1/DI[3]
CARRY4 (Prop_carry4_DI[3]_CO[3])		0.396	13.746 r	acc_reg[24]_i_1/CO[3]
net (fo=1, unplaced)		0.000	13.746	acc_reg[24]_i_1_n_0
			r	acc_reg[28]_i_1/CI
CARRY4 (Prop_carry4_CI_O[1])		0.337	14.083 r	acc_reg[28]_i_1/O[1]
net (fo=1, unplaced)		0.000	14.083	acc_reg[28]_i_1_n_6
FDRF			r	acc_reg[29]/D
-----				
(clock axis_clk rise edge)				
		12.000	12.000 r	
net (fo=0)		0.000	12.000 r	axis_clk (IN)
		0.000	12.000	axis_clk
			r	axis_clk_IBUF_inst/I
IBUF (Prop_ibuf_l_0)		0.838	12.838 r	axis_clk_IBUF_inst/O
net (fo=1, unplaced)		0.760	13.598	axis_clk_IBUF
			r	axis_clk_IBUF_BURF_inst/I
BURF (Prop_burf_l_0)		0.091	13.689 r	axis_clk_IBUF_BURF_inst/O
net (fo=145, unplaced)		0.439	14.128	axis_clk_IBUF_BURF
FDRF			r	acc_reg[29]/C
clock pessimism		0.184	14.311	
clock uncertainty		-0.035	14.276	
FDRF (Setup_fdrf_C_D)		0.076	14.352	acc_reg[29]
-----				
required time			14.352	
arrival time			-14.083	
-----				
slack			0.269	


## Simulation Waveform:

- Coefficient program, and read back

 


從波形圖可以看到先對 fir 設定 data length 跟 coefficient，然後再把 coefficient 讀出來。接著 program ap\_start，fir 開始計算之後 fir\_tb 會持續 polling ap\_done。

- Data-in stream-in

 


可以看到 fir 每 11 個週期會讀入 1 筆資料

- Data-out stream-out

 

可以看到 fir 每 11 個週期會輸出 1 筆資料

- RAM access control

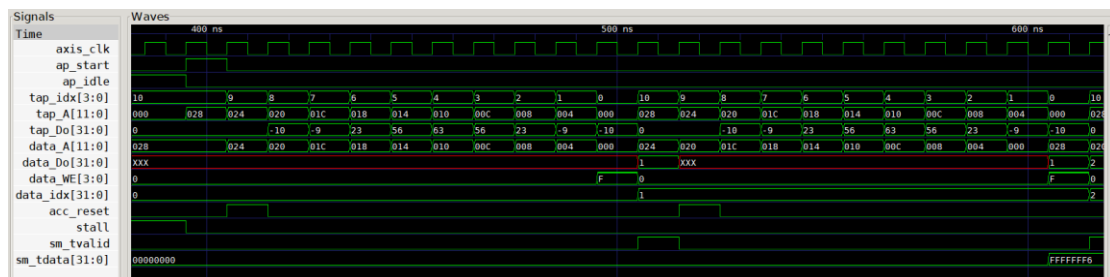

- FSM

無 FSM

## Simulation result

```
===== setup phase =====
---Start the coefficient input(AXI-lite)---
Check Coefficient ...
OK: exp =      0, rdata =      0
OK: exp =    -10, rdata =    -10
OK: exp =     -9, rdata =     -9
OK: exp =     23, rdata =     23
OK: exp =     56, rdata =     56
OK: exp =     63, rdata =     63
OK: exp =     56, rdata =     56
OK: exp =     23, rdata =     23
OK: exp =     -9, rdata =     -9
OK: exp =    -10, rdata =    -10
OK: exp =      0, rdata =      0
Tap programming done ...
---End the coefficient input(AXI-lite)---
```

所有係數都正確

```

[PASS] [Pattern      594] Golden answer:      -1630, Your answer:      -1630
[PASS] [Pattern      595] Golden answer:      -1647, Your answer:      -1647
[PASS] [Pattern      596] Golden answer:      -1464, Your answer:      -1464
[PASS] [Pattern      597] Golden answer:      -1281, Your answer:      -1281
[PASS] [Pattern      598] Golden answer:      -1098, Your answer:      -1098
OK: exp =          0, rdata =          0
-----End the data input(AXI-Stream)-----
[PASS] [Pattern      599] Golden answer:      -915, Your answer:      -915
ap_done sampled
OK: exp =          4, rdata =          4
-----Congratulations!-----
-----Simulation2-----
-----  ^ ^  PASS  ^ ^  -----
-----
Total cycle count = 6610

```

所有 output 跟 golden 相同

計算 600 筆資料共花費 6610 個 clock cycle